

Computer architecture project

Create a microprocessor



Team members:

Mohamed Taha Salah	192000280
Abdulrahman Gaber	192000272
Salwa Hisham Ismail	192000277
Mohamed Heshmat	192000255


Submitted to:

DR: Amr Zamel
TA: Nancy El Arabawy

Introduction:

It is required to design and build a simple processor (non- pipelined) with all the components introduced throughout computer architecture course, size of instruction = 16 bits

CPU Content:

 

CPU: The central processing unit (CPU) is that portion of a computer that fetches and executes instructions. It consists of an ALU, control unit and registers in a system with a signal processing unit.


ALU: arithmetic and logic unit (ALU), which performs simple arithmetic and logical operations.

Register: a register file is an array of processor registers in a central processing unit.

Control unit: all computer operations are controlled by the control unit.

CPU Connection:

 The processor contains a single general-purpose register called an accumulator (AC), a Program Counter (PC), a Memory Address Register (MAR) and a Memory Buffer Register (MBR), Instruction register (IR).




Fetch Cycle

1. Instruct stored into pc.
2. Pc sends it to MAR.
3. MAR sends the address to the main memory.
4. Main memory sends content of address to MDR.
5. MDR sends address content to IR.
6. Pc increment by one.

Execute Cycle:

1. IR sends the location that stores in ROM to MAR.
2. Accumulator sends content of address to ALU.
3. All of this happened under management of the control unit.


Input / Output Connection:

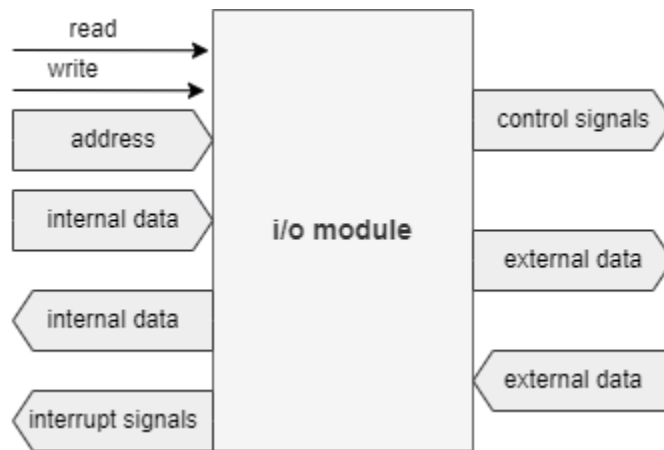

Main memory:

Data memory: (ROM) read the instruction.

 Instruction memory: (RAM) stores the instructions of a program given an address.



Memory Constraints:

Instructions >>>>> 16 Bit

Number of instructions >>>>> 16

Opcode >>>>> 4 Bit

Address >>>>> 12 Bit

Data >>>>> 16 Bit

Opcode (binary)	operation
0000	Load AC from memory
0001	Store AC into memory
0010	Add to AC from memory, Result in AC
0011	Subtract memory from AC, Result in AC
0100	Logical AND memory and AC , Result in AC
0101	Logical OR memory and AC , Result in AC
0110	Logical XOR memory and AC , Result in AC
0111	Logical NOT memory , Result in AC
1000	Logical SHL memory , Result in AC
1001	Logical SHR memory , Result in AC
1010	Logical ROL memory , Result in AC
1011	Logical ROR memory , Result in AC
1100	MOV memory int AC, Result in AC
1101	Increment memory , Result in AC
1110	Decrement memory , Result in AC
1111	Reset memory , Result in AC

Main Memory (RAM):

Address (Hexa decimal)	Content
E2E	0002
E2F	0001
E30	0008
E31	0007
E32	0005
E33	0003
E34	0F0F
E35	000A
E36	0000

Instructions in (ROM):

Index	Instructions
0	0E2E
1	2E35
2	3E30
3	1E32
4	DE32
5	1E2F
6	EE2F
7	1E33

